

# Electrical Theory

## Power Flow on AC Transmission Lines


PJM State & Member Training Dept.

At the completion of this training, the learner will be able to:

- Describe the basic make-up and theory of an AC transmission line
- Given the formula for real power, calculate reactive power flow on an AC transmission facility
- Given the formula for reactive power, calculate reactive power flow on an AC transmission facility
- Given voltage magnitudes and phase angle information between 2 busses, determine how real and reactive power will flow

# AC Power Flow

# AC Power Flow Overview

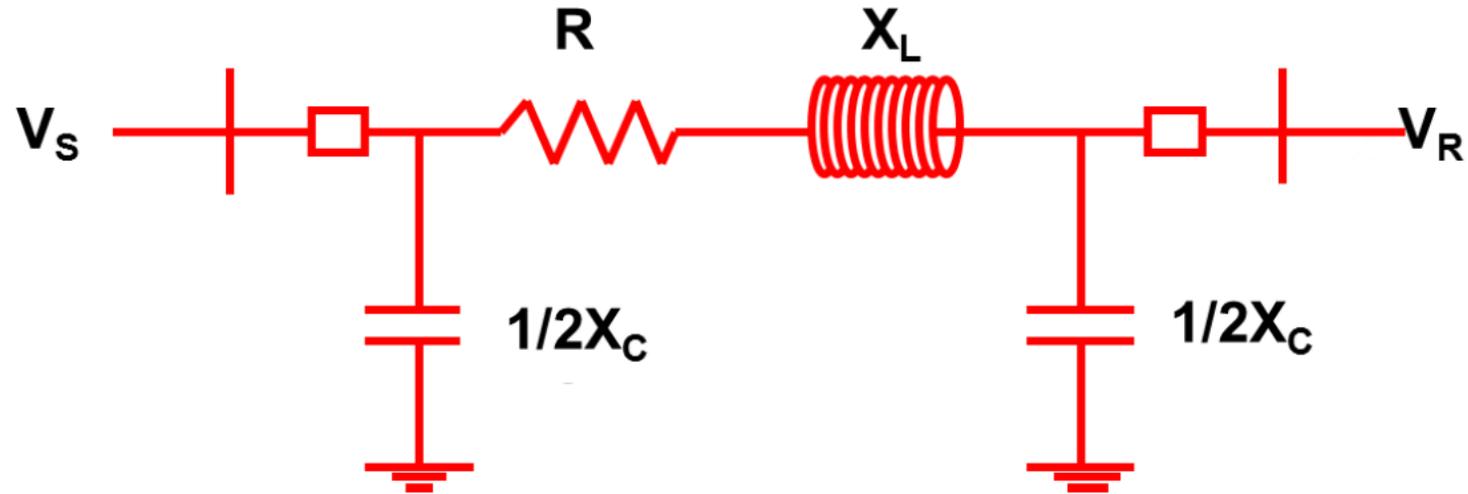

- Different lines have different values for  $R$ ,  $X_L$ , and  $X_C$ , depending on:
  - Length
  - Conductor spacing
  - Conductor cross-sectional area
- $X_C$  is equally distributed along the line

# Power in Out-of-Phase AC Circuits

- Inductance and capacitance depend on:
  - Conductor cross-sectional area
  - Conductor length
  - Distance between phase conductors
- Inductive reactance:
  - Decreases as the cross-sectional area of the conductor increases
  - Increases as the conductor spacing increases
- Capacitive reactance:
  - Increases as the cross-sectional area of the conductor increases
  - Decreases as the conductor spacing increases

# Power in Out-of-Phase AC Circuits

- Capacitance is always greater for underground cables where conductors and ground are very close
- AC voltage causes the charge on the conductors to increase and decrease as the voltage increases and decreases
- **Charging Current** is current that flows due to the alternate charge and discharge of the line due to alternating voltage regardless of whether the circuit is closed or open-ended

# Review

- Total impedance ( $Z$ ) is made up of resistance, inductance, and capacitance
- The reactive component ( $X$ ) of impedance is made up of inductance and capacitance and is greater than the resistive ( $R$ ) component of a line
- The Reactive components magnitude correlate with the voltage level

# Real Power Flow

# Power Flow

- MW flow on a transmission facility is the result of the resistive component (R)
  - Real power is measured in watts (W) and is in-phase with the load
- VAR flow on a transmission facility is the result of the reactive component (X)
  - Reactive power is measured in volt amperes reactive (VAR) and is out of phase with the load
- VARs supply magnetizing current for inductive loads and charging current for capacitive loads

# Real Power Flow

Real Power ( $P_R$ ) flow between two buses is obtained by:

$$P_R = \frac{V_S \times V_R}{X} \times \sin \delta$$

Where,

$P$  = Real power in MW

$V_S$  = Sending-end voltage

$V_R$  = Receiving-end voltage



$X$  = Line reactance between buses

$\delta$  = Angle delta between bus voltages

# Real Power Flow

- Angle theta,  $\theta$  is the symbol for the angle difference between current and voltage
  - Used in determining power factor indicating the portion of total current and voltage that is producing real power
- Angle delta,  $\delta$  is the symbol for phase angle difference between the sending and receiving voltages
  - Negative MW's indicate flow into the sending bus Positive MW's indicate flow out of the sending bus

# Real Power Flow

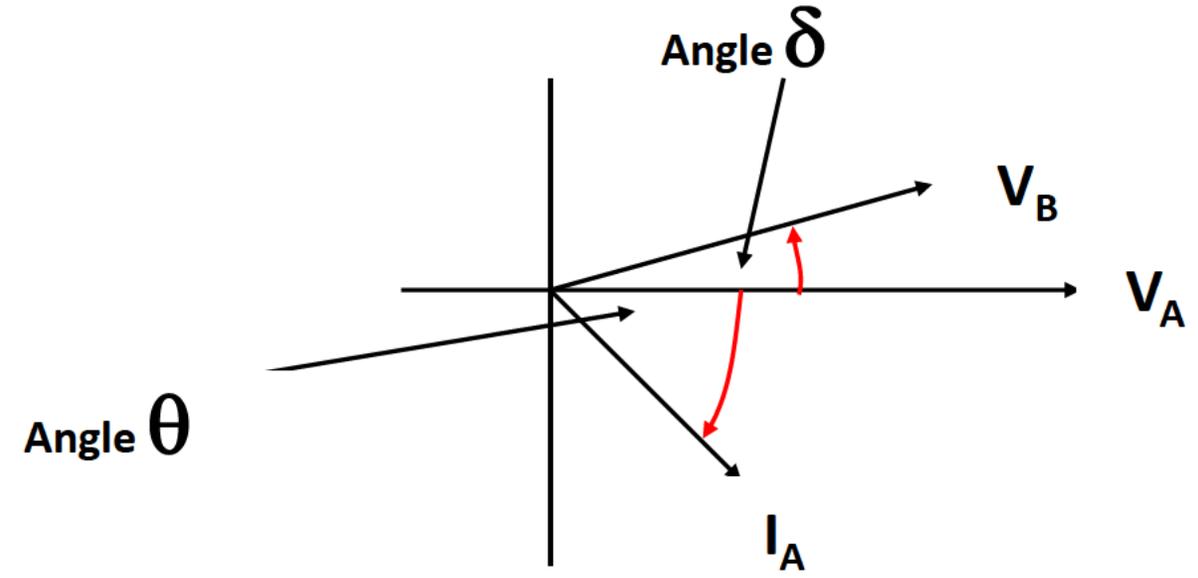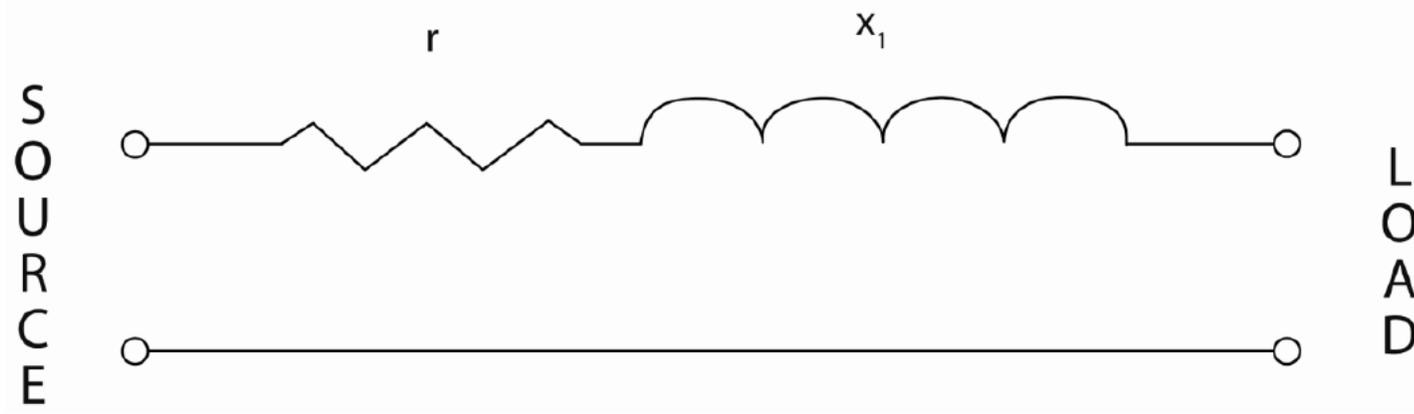

Angular difference between buses

# Real Power Flow

- In order to transfer real power across a transmission line, there must be an angle ( $\delta$ ) between the voltages at each end of the line
- Greater phase angle difference; more real power transferred
- Maximum power transfer theoretically occurs at  $90^\circ$
- Real Power flows “downhill” to a more lagging angle

# Flow of Real Power Summary

- Increasing reactance results in a decrease in real power transfer
- Increasing the phase angle difference increases real power transfer
- Neither increasing or decreasing voltage magnitudes has a significant effect on the flow of real power
- If impedances of parallel lines are equal, power flow is equally distributed
- If impedances of parallel lines are different, real power flow is inversely proportional to line impedance

# Reactive Power Flow

# Flow of Reactive Power

- Reactive Power ( $P_Q$ ) flow on a transmission line is a result of the inductive reactance of the load requirement and is obtained by:

$$P_Q = \left\{ \frac{(V_S)(V_S - V_R)}{X} \right\} \cos \delta$$

Where,

Q = Reactive Power in MVAR

$V_S$  = Sending-end voltage

$\Delta V$  = Difference between bus voltages  $V_S$  and  $V_R$

X = Line reactance between buses

$\delta$  = Phase angle between  $V_S$  and  $V_R$

# Flow of Reactive Power

- VARS flow only if there is a difference in bus voltage potential
- VAR's flow downhill from a higher per unit value to a lower per unit value of voltage
- Reactive power flow is similar to real power flow:
  - Negative VAR value indicates flow into the reference bus
  - Positive VAR value indicates flow out of the reference bus




# Flow of Reactive Power Summary

- Increasing the voltage magnitude at the sending end increases the reactive power flow toward the receiving end
- Increasing the voltage magnitude at the receiving end decreases the reactive power flow toward the receiving end
- Increasing the path reactance between the two buses decreases the reactive power flow towards the receiving end

# Integrating Real & Reactive Power Flows
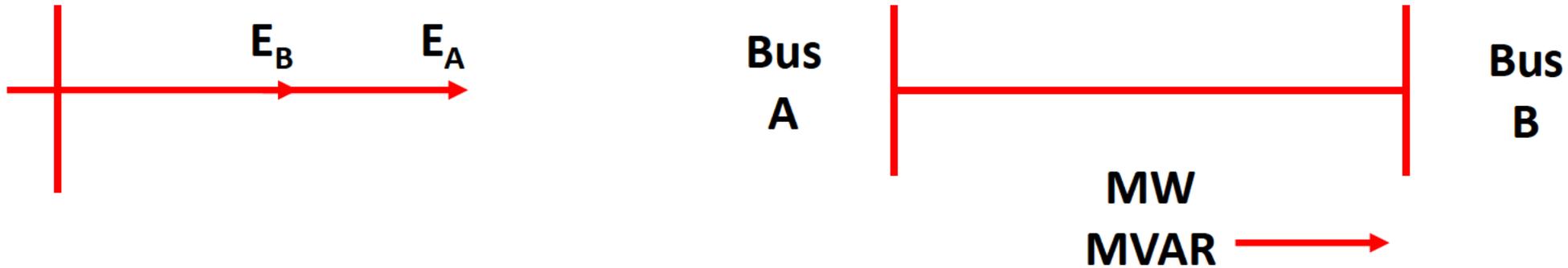
# Scenario 1


- Voltages are in-phase; Bus A voltage > Bus B voltage



- No MW flow; no phase angle difference
- VAR's flow from Bus A to Bus B
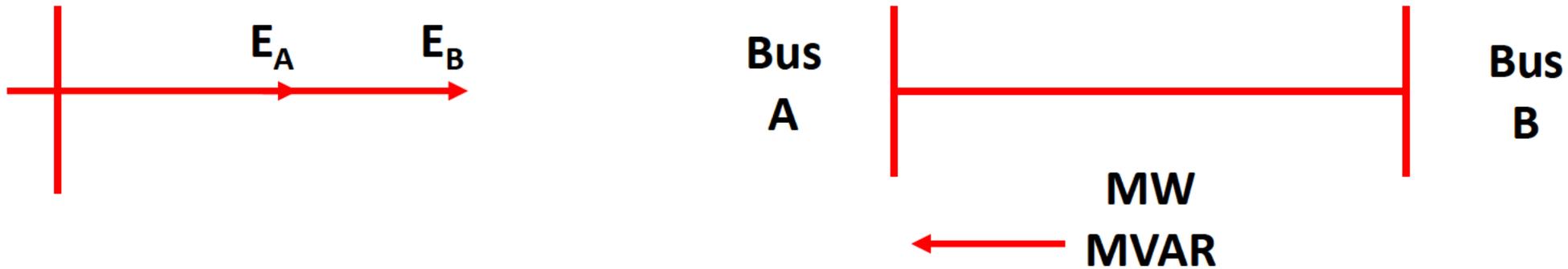
## Scenario 2


- Voltages are in-phase; Bus A voltage < Bus B voltage



- No MW flow; no phase angle difference
- VAR's flow from Bus B to Bus A
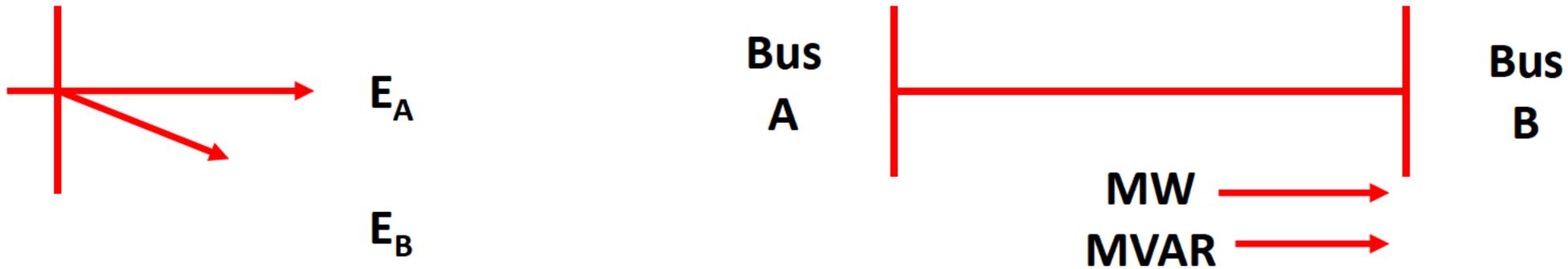
## Scenario 3


- Voltages are not in-phase; Bus A voltage > Bus B voltage



- MW flow; Bus B voltage is lagging Bus A voltage
- VAR's flow from Bus A to Bus B
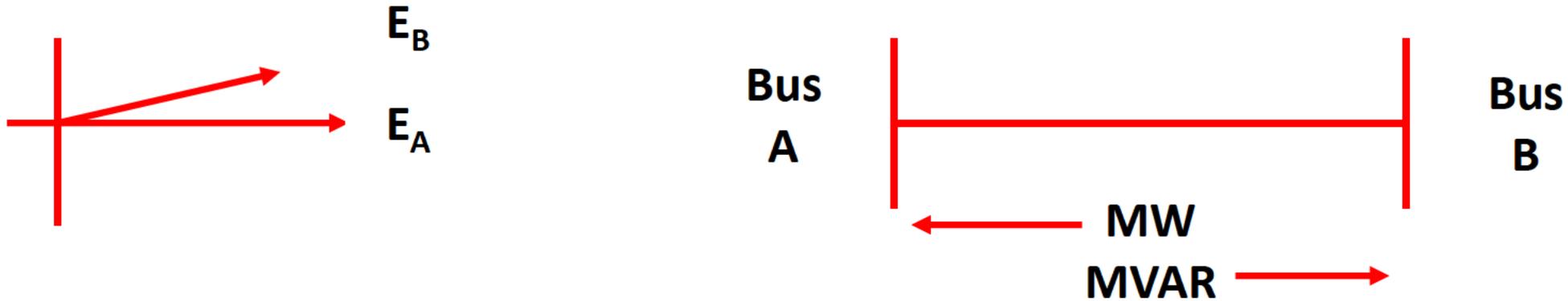
## Scenario 4


- Voltages are not in-phase; Bus A voltage > Bus B voltage



- MW flow; Bus A voltage is lagging Bus B voltage
- VAR's flow from Bus A to Bus B
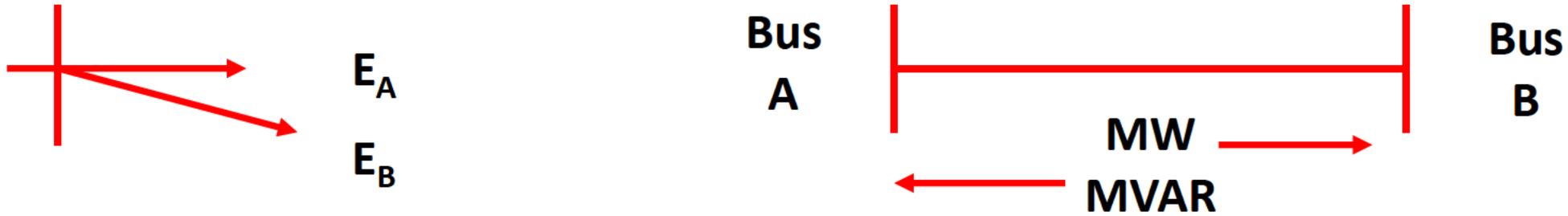
## Scenario 5


- Voltages are not in-phase; Bus A voltage < Bus B voltage



- MW flow; Bus B voltage is lagging Bus A voltage
- VAR's flow from Bus B to Bus A
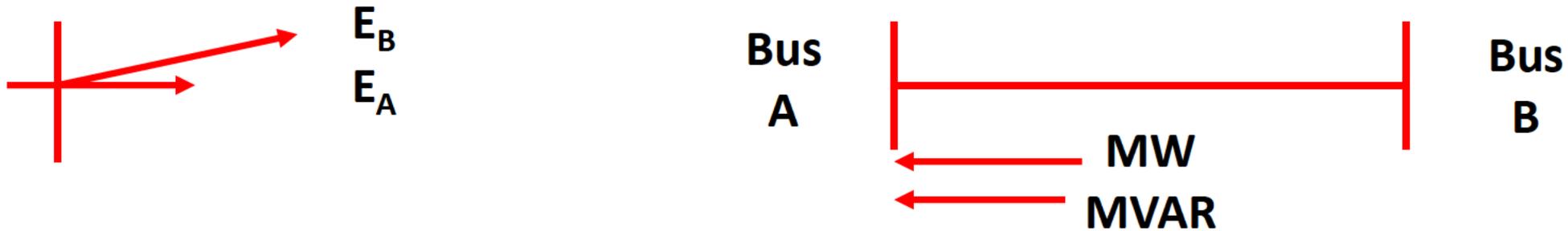
## Scenario 6


- Voltages are not in-phase; Bus A voltage < Bus B voltage



- MW flow; Bus A voltage is lagging Bus B voltage
- VAR's flow from Bus B to Bus A
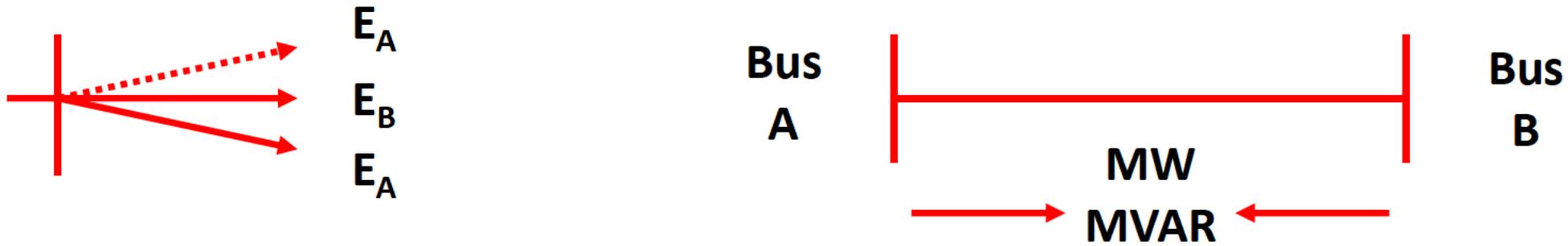
# Scenario 7

- Voltages are not in-phase; Bus A voltage = Bus B voltage



- MW flow
  - Bus A voltage lags Bus B voltage, MW flow into Bus A
  - Bus B voltage lags Bus A voltage, MW flow out of Bus A
- VAR's flow from Bus B and from Bus A into the line

# Questions?

**PJM Client Management & Services**

**Telephone: (610) 666-8980**

**Toll Free Telephone: (866) 400-8980**

**Website: [www.pjm.com](http://www.pjm.com)**



**The Member Community is PJM's self-service portal for members to search for answers to their questions or to track and/or open cases with Client Management & Services**

# Resources & References



Miller, R. & Malinowski, J. (1994). *Power System Operation*. Boston, MA. McGraw-Hill

Rustebakke, H.M. (Ed) (1983). *Electric Utility Systems & Practices*. 4<sup>th</sup> edition, Wiley Interscience